



Verification
Futures
2025

Static Sign-Off Methodologies:

Liberating Functional Verification from Boolean Shackles


Prakash Narain

November 12, 2025

Early functional verification & sign-off



 Avoid costly RTL & netlist ECOs/iterations




Simulation & formal: Boolean analysis




Early RTL design needs a different approach

Static sign-off: Minimally Boolean


Liberated from
Boolean shackles

 


Static sign-Off: Abstract checking

 

 
Static sign-off: Starts at early RTL design




Static sign-off rule configurability

 


Expanding static sign-off applications

 

Advanced static sign-off methodologies

 

RTL Linting Sign-Off

 

1 High value rules

```
always @(en1 or en2)
begin
    if ( en1 )
        out1 = 2'b00;
    if ( en2 )
        out1 = 2'b11;
end
```

Explicitly define intent

```
always @(en1 or en2)
```

```
begin
```

```
    if ( en1 )
```

```
        out1 = 2'b00;
```

```
    if ( en2 )
```

```
        out1 = 2'b11;
```

```
end
```

Use “always_<spec>” to
explicitly define intent

Explicitly define intent

always_comb

begin

if (en1)

out1 = 2'b00;

if (en2)

out1 = 2'b11;

end

“always_comb” explicitly
specifies combinational logic

Don't use multiple sequential conditionals

```
always_comb
```

```
begin
```

```
    out1 = 1'b10;
```

```
    if ( en1 )
```

```
        out1 = 2'b00;
```

```
    if ( en2 )
```

```
        out1 = 2'b11;
```

```
end
```

Use if/then/else when there are multiple sequential conditional assigns

Don't use multiple sequential conditionals

```
always_comb  
begin  
    if ( en2 )  
        out1 = 2'b11;  
    else if ( en1 )  
        out1 = 2'b00;  
    else  
        out1 = out1  
    end
```

Clarifies that only 1 assign will be applied

Indentation aligns with construct

```
always_comb
begin
    if ( en2 )
        out1 = 2'b11;
    else if ( en1 )
        out1 = 2'b00;
    else
        out1 = out1;
end
```


Indentation must align with construct

Indentation aligns with construct



```
always_comb  
begin  
    if ( en2 )  
        out1 = 2'b11;  
    else if ( en1 )  
        out1 = 2'b00;  
    else  
        out1 = out1;  
end
```

Indentation corrected

2 Multi-policy linting

 

3 Targeted debug

  

Grouping violations

Advanced RTL linting sign-off



High value rules




Target debug




Multipolicy runs

CDC Sign-Off

 


1 CDC glitch analysis

 

1 CDC glitch analysis




“Do not touch” MUXes

 


Netlist-level
glitch CDC sign-off

2 Dynamic CDC verification

 

Correlation loss


2 Dynamic CDC verification

 

Advanced CDC sign-off



Structural sign-off

 


Glitch
checking




Dynamic
CDC
verification


RDC Sign-Off

 


Reset domain crossing sign-off

 


Increasing use of asynchronous resets

 


RDC key differences from CDC

 

 
1 RDC errors can occur in same clock domain




2 RDC sign-off requires global analysis

 

2 CDC sign-off only needs local analysis

 


 3 RDC-specific analysis needed for sign-off




4 RDC errors have lower frequency

 
RDC: Source flop change rate:
event dependent




CDC: Source flop change rate:
~ 0.1 GHz

 


RDC error: Metastability

 

 
RDC error: Improper functional correlation



RDC error: Glitches

 


Low-noise violation reports critical

 



Noisy Report

VS.

 

Low Noise Report

Reset scenarios reduce noise

  


Efficient debug




Advanced RDC sign-off methodology



Low-noise

 


Functional analysis

 

Hierarchical flow


DFT Sign-Off

 

Advanced DFT static sign-off


Controllability

Can you drive it?

 


Observability

Can you see it?

 


1 Use comprehensive rulesets

 


RULE: Sequential capture depth through non-scan flip-flops should not exceed user-specified limit

1 Use comprehensive rulesets

 


RULE: A test clock should not fan out and reconverge with itself

2 Utilize fine-grained rules

 


RULE 1: Asynchronous reset convergence glitch

 


RULE 2: Asynchronous reset reconvergence glitch

2 Utilize fine-grained rules

 


RULE: Asynchronous reset convergence glitch

2 Utilize fine-grained rules

 


RULE: Asynchronous reset convergence glitch

2 Utilize fine-grained rules

 


RULE: Two or more test clocks should not converge while driving a flip-flop's clock input


3 Analyze all test modes in one run

 


3 Analyze all test modes in one run

 

One set-up
hours vs weeks

 


Fast runtime
2 min/M gates/mode

 


Consolidated
hierarchical reports

4 Group errors by root cause

 


RULE: No clock glitch can reach destination flip-flops through convergence point


5 Deploy at all design stages

 

6 Leverage multi-vendor DFT flows

 

Advanced DFT sign-off

 

Comprehensive,
fine-grained rules




Multimode
tests




Root cause
grouping


Connectivity Sign-Off

 


Connectivity static sign-off

 


1 Efficient rule definition

 


1 Efficient rule definition

 

 
1 Efficient rule creation, tiered checking



 
1 Efficient rule creation, tiered checking



2 Start connectivity sign-off early

 


2 Check abutment connectivity early

 


Allowed Arcs =
 $\{ A B \} \{ A C \} \{ * TOP \}$


3 Glitch checking

 


Static sign-off vs. Formal

 

Static sign-off vs. Simulation

 


Static sign-off vs. Simulation

 

Advanced connectivity sign-off



Efficient rule
definition

 


Speed for
RTL sign-off




Create groups


Hardware Security Sign-Off

 


Eliminate HW security vulnerabilities

 


Spectre stale data leak

 


1 Data integrity

 

2 Leakage prevention

 


3 Interference safeguarding

 


User-defined + general rules



Static sign-off vs. Formal verification

 

Hardware security sign-off

 

Comprehensive
analysis



User-defined
& general rules



RTL designers
need speed

Static Sign-Off Suite

